

VTŠ: Osnovi računarske tehnike

Bulova algebra

mr. Veličković Zoran
Mart, 2010.

Bulova algebra

- ❑ Oko 1850, Britanski matematičar **George Boole** (1815–1864), je razvio novu formu matematike koja je poznata kao *Bulova algebra*.
- ❑ Bulova algebra je jedan od alata koji se koriste u dizajniranju elektronskih kola od kojih su sačinjeni računarski sistemi.
- ❑ Osnovna načela Bulove algebre su:
 - Logički iskaz može imati samo **tačnu** (TRUE) ili **netačnu** vrednost (FALSE).
 - Logički iskazi se mogu kombinovati na razne načine. Ako se iskazi kombinuju I (AND) operatorom nazivaju se **konjunkcije**.
 - Iskazi kombinovani ILI (OR) operatorom nazivaju se **disjunkcije**.
- ❑ Veza između logičkih iskaza može biti prikazana simboličkom logikom putem **jednačina** ili **tablicom istinitosti**.

Bulova algebra



Operatori u Bulovoj algebri

- Tek je Shannon, koncept Bulove algebre (TRUE-FALSE), primenio na binarne vrednosti **0** i **1**, koje se jednostavno mogu realizovati elektronskim kolima.
- Logičke funkcije se mogu predstaviti **grafičkim simbolima, jednačinama** ili **tablicom istinitosti**.
- Simboli **&**, **|**, **^** i **-** se koriste da predstave:
 - I (AND),
 - ILI (OR),
 - ISKLJUČIVO ILI (XOR)
 - NEGACIJU (NOT), (horizontalna linija).

Prikaz osnovnih logičkih funkcija

jednačina


Tablica istinitosti

Grafički-
Logičkim
kolima

Alternativa

$$y = a$$


a	y
0	0
1	1

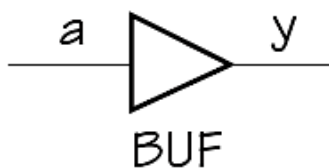

$$y = a$$

$$y = a \& b$$


a	b	y
0	0	0
0	1	0
1	0	0
1	1	1

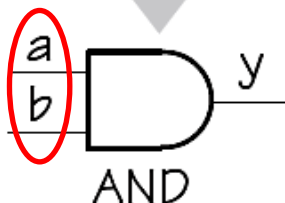

$$y = a \cdot b$$

$$y = a | b$$


a	b	y
0	0	0
0	1	1
1	0	1
1	1	1

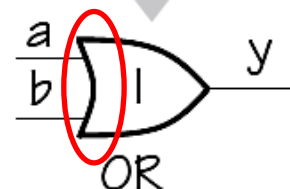

$$y = a + b$$

$$y = a \wedge b$$

a	b	y
0	0	0
0	1	1
1	0	1
1	1	0

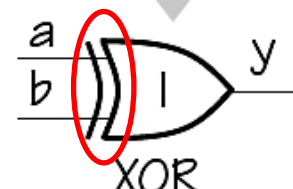

$$y = a \oplus b$$

Prikaz osnovnih logičkih funkcija (2)


jednačina

$$y = \bar{a}$$

Tablica istinitosti

a	y
0	1
1	0

Logičkim kolima

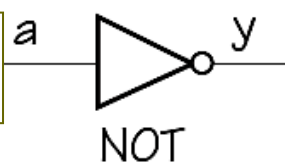


Alternativa

$$y = a'$$


$$y = \overline{a \& b}$$

a	b	y
0	0	1
0	1	1
1	0	1
1	1	0

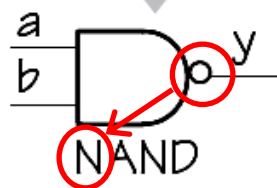


$$y = \overline{a \mid b}$$

a	b	y
0	0	1
0	1	0
1	0	0
1	1	0


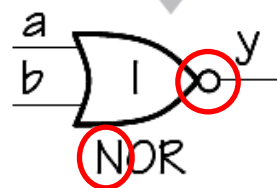


$$y = \overline{a \wedge b}$$

a	b	y
0	0	1
0	1	0
1	0	0
1	1	1


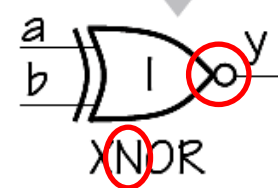


Specijalni slučajevi funkcija (1)

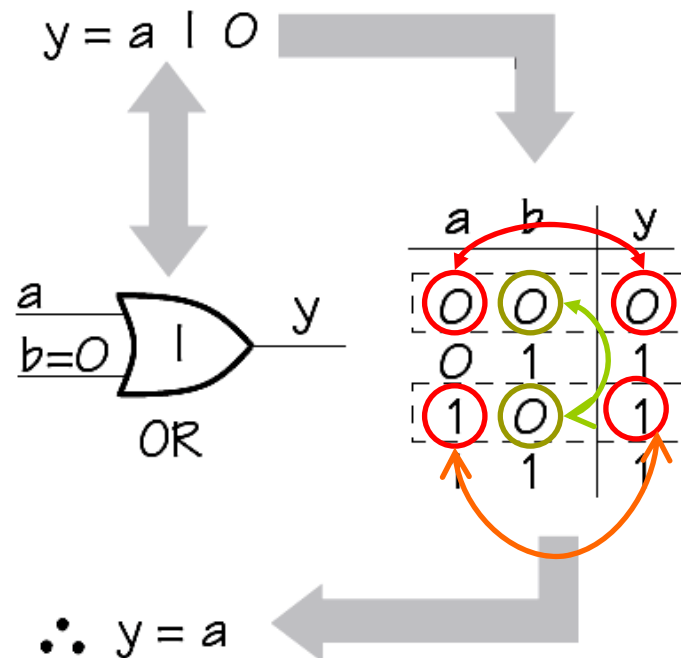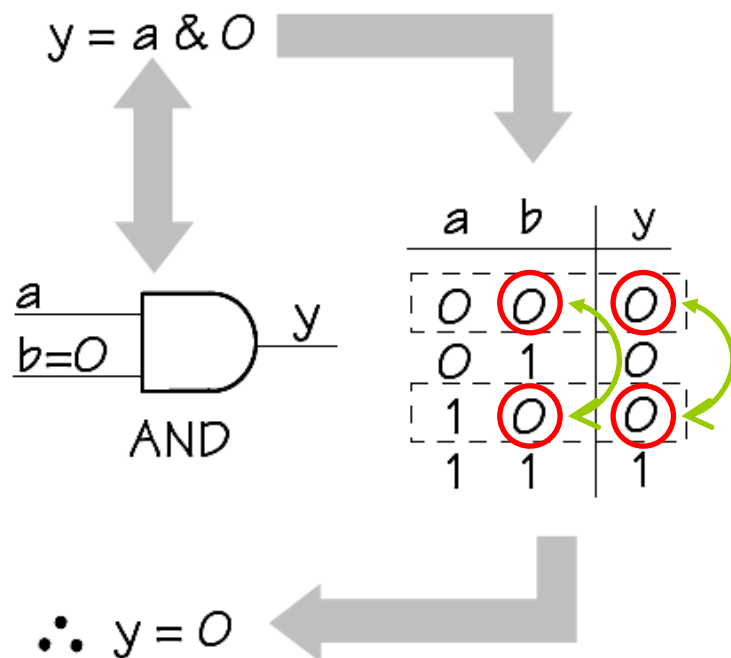



ZAPAMTITE !!

Specijalni slučajevi funkcija (2)

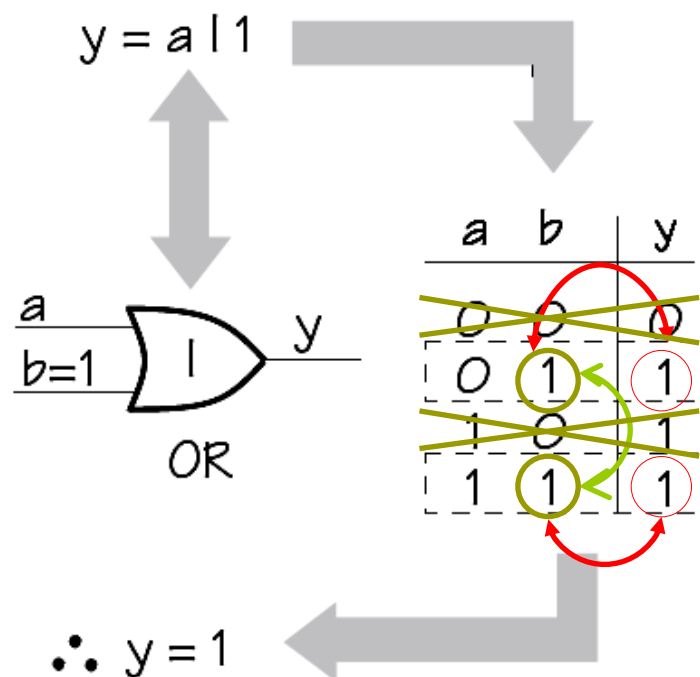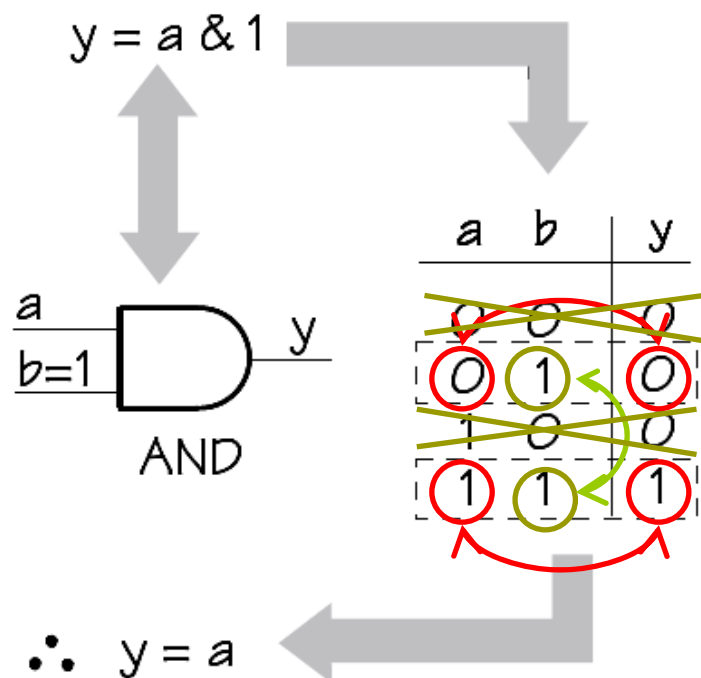



ZAPAMTITE !!

Specijalni slučajevi funkcija (3)

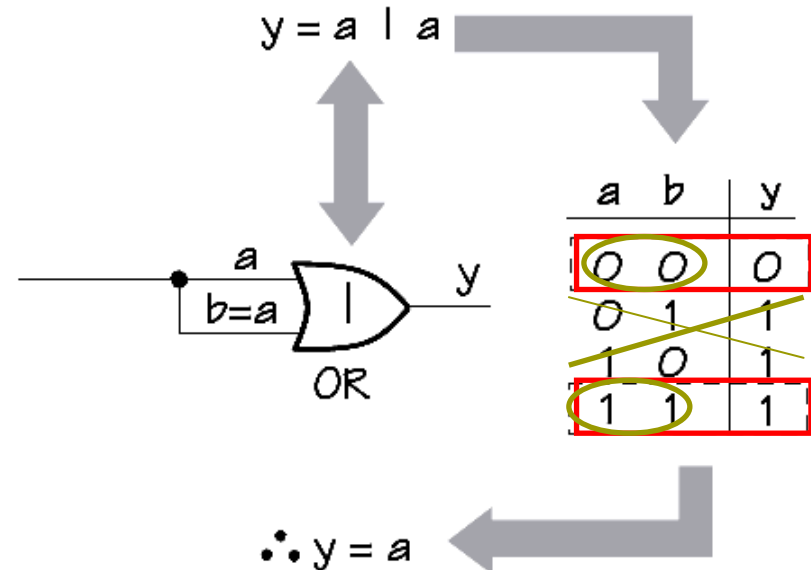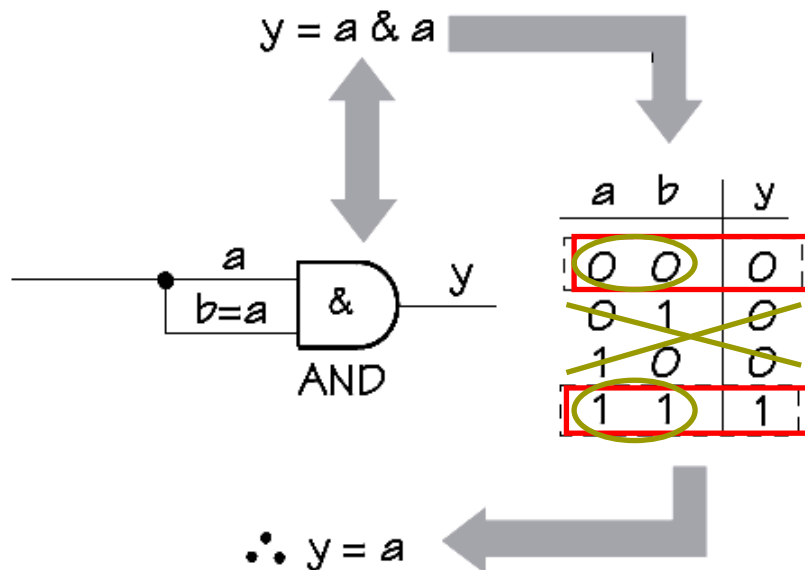


ZAPAMTITE !!

Komplementiranje

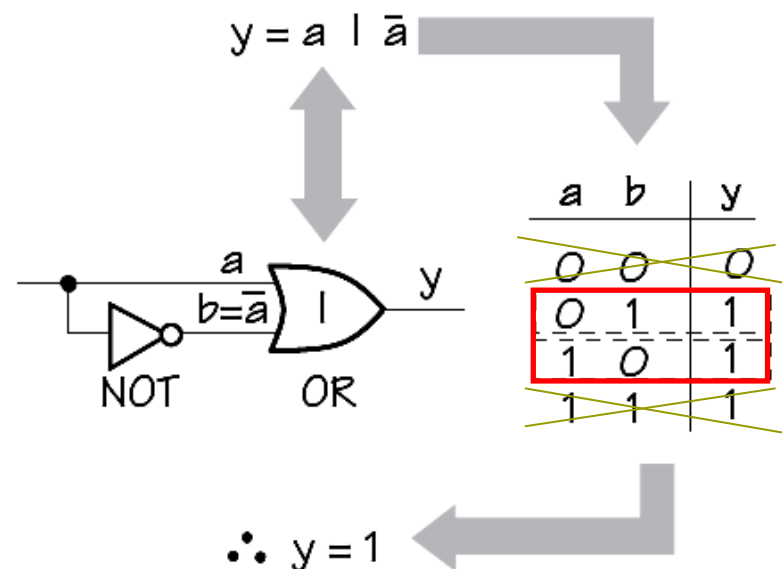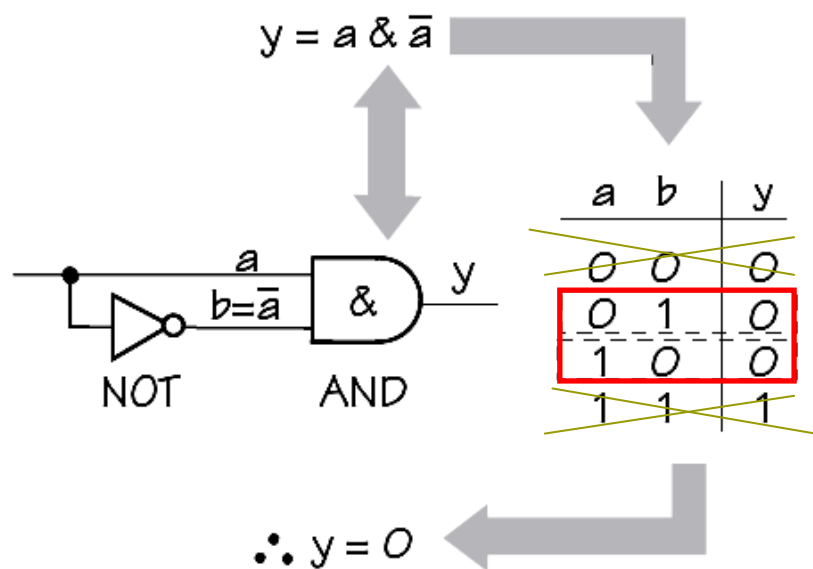


ZAPAMTITE !!

Negacija

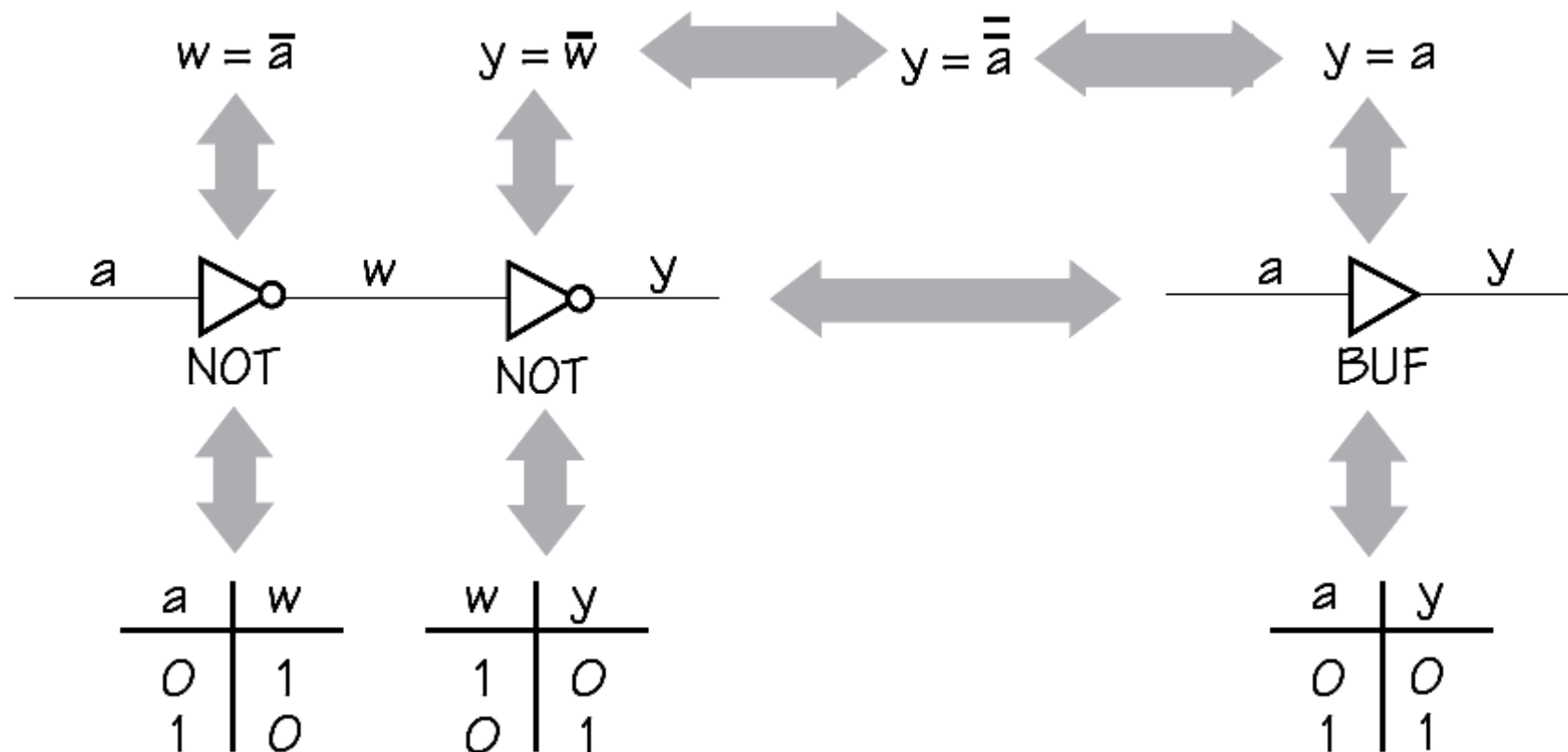


ZAPAMTITE !!

Osobina komutacije

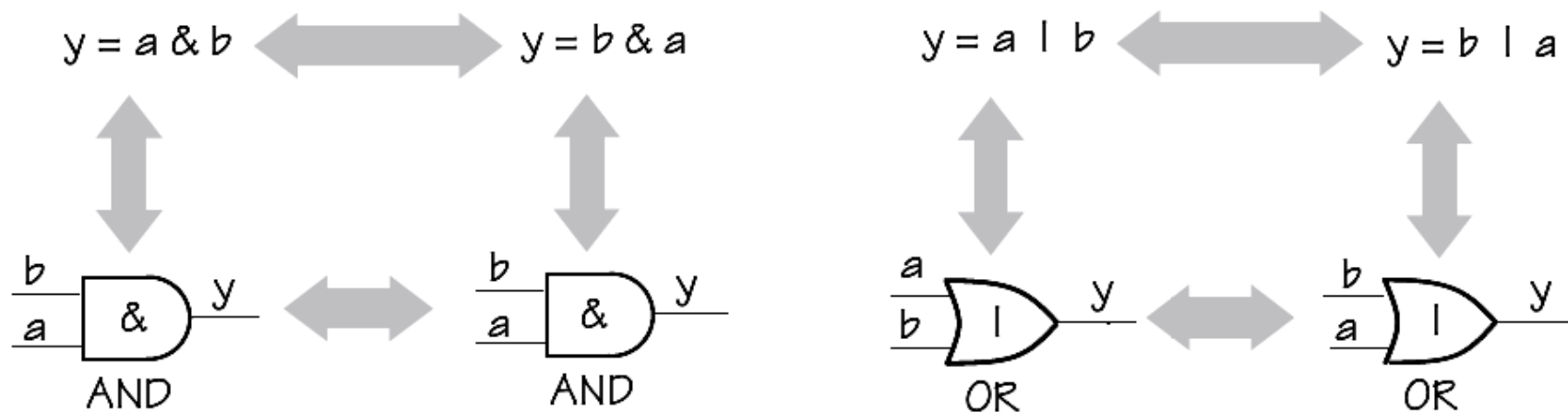


Osobina asocijativnosti

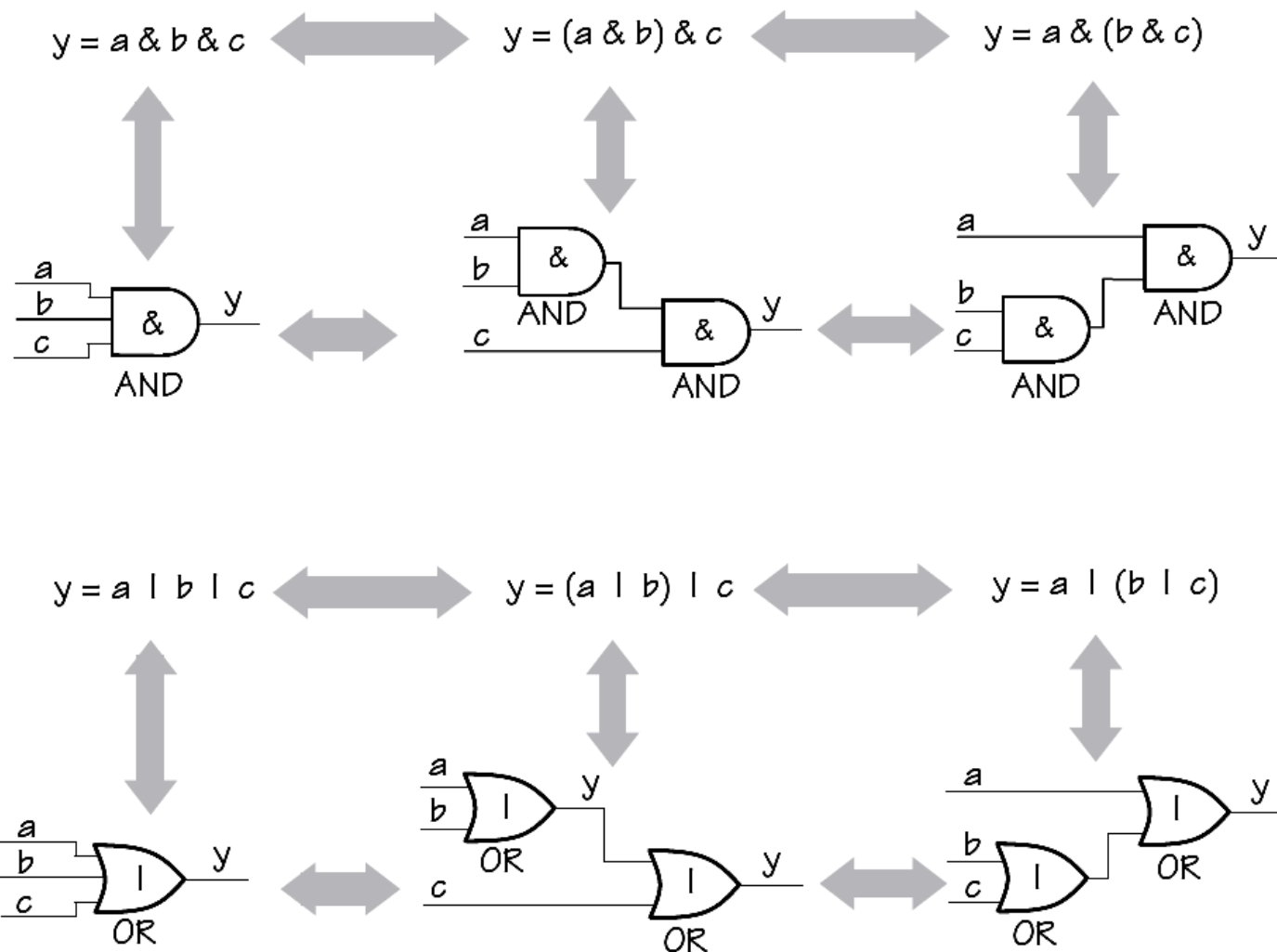


Osnovne jednakosti u Bulovoj algebri

Table 13.11 Rules of Boolean algebra

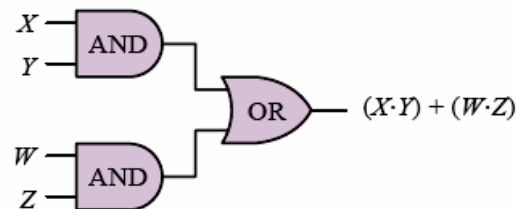1. $0 + X = X$
2. $1 + X = 1$
3. $X + X = X$
4. $X + \bar{X} = 1$
5. $0 \cdot X = 0$
6. $1 \cdot X = X$
7. $X \cdot X = X$
8. $X \cdot \bar{X} = 0$
9. $\bar{\bar{X}} = X$
10. $X + Y = Y + X$
11. $X \cdot Y = Y \cdot X$
12. $X + (Y + Z) = (X + Y) + Z$
13. $X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$
14. $X \cdot (Y + Z) = X \cdot Y + X \cdot Z$
15. $X + X \cdot Z = X$
16. $X \cdot (X + Y) = X$
17. $(X + Y) \cdot (X + Z) = X + Y \cdot Z$
18. $X + \bar{X} \cdot Y = X + Y$
19. $X \cdot Y + Y \cdot Z + \bar{X} \cdot Z = X \cdot Y + \bar{X} \cdot Z$



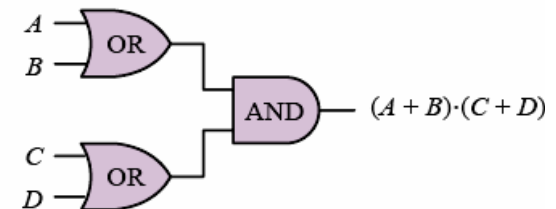Sum of products
expression
 $(X \cdot Y) + (W \cdot Z)$



Product of sums
expression
 $(A + B) \cdot (C + D)$

Figure 13.18 Sum-of-products and product-of-sums logic functions

} Commutative law

} Associative law

Distributive law

Absorption law

Uprošćavanje log. iskaza

Problem

Using the rules of Table 13.11, simplify the following function using the rules of algebra.

$$f(A, B, C, D) = \overline{A} \cdot \overline{B} \cdot D + \overline{A} \cdot B \cdot D + B \cdot C \cdot D + A \cdot C \cdot D$$

Solution

Find: Simplified expression for logical function of four variables.

Analysis:

$$\begin{aligned} f &= \overline{A} \cdot \overline{B} \cdot D + \overline{A} \cdot B \cdot D + B \cdot C \cdot D + A \cdot C \cdot D \\ &= \overline{A} \cdot D \cdot (\overline{B} + B) + B \cdot C \cdot D + A \cdot C \cdot D && \text{Rule 14} \\ &= \overline{A} \cdot D + B \cdot C \cdot D + A \cdot C \cdot D && \text{Rule 4} \\ &= (\overline{A} + A \cdot C) \cdot D + B \cdot C \cdot D && \text{Rule 14} \\ &= (\overline{A} + C) \cdot D + B \cdot C \cdot D && \text{Rule 18} \\ &= \overline{A} \cdot D + C \cdot D + B \cdot C \cdot D && \text{Rule 14} \\ &= \overline{A} \cdot D + C \cdot D \cdot (1 + B) && \text{Rule 14} \\ &= \overline{A} \cdot D + C \cdot D = (\overline{A} + C) \cdot D && \text{Rules 2 and 6} \end{aligned}$$

Prioritet Bulovih operatora

- Prioritet operatora u Bulovoj algebri je sličan kao kod standardne aritmetike:


$$6 + 2 \times 4 \equiv 6 + (2 \times 4)$$

$$a \mid b \& c \equiv a \mid (b \& c)$$


- Usled ove sličnosti & (AND) operator se naziva **logičko množenje** ili *proizvod*, dok je $\mid$ (OR) operator poznat kao **logičko sabiranje** ili *suma*.

$$6 \times (5 + 2) \equiv (6 \times 5) + (6 \times 2)$$


Logičko (Bulovo) množenje

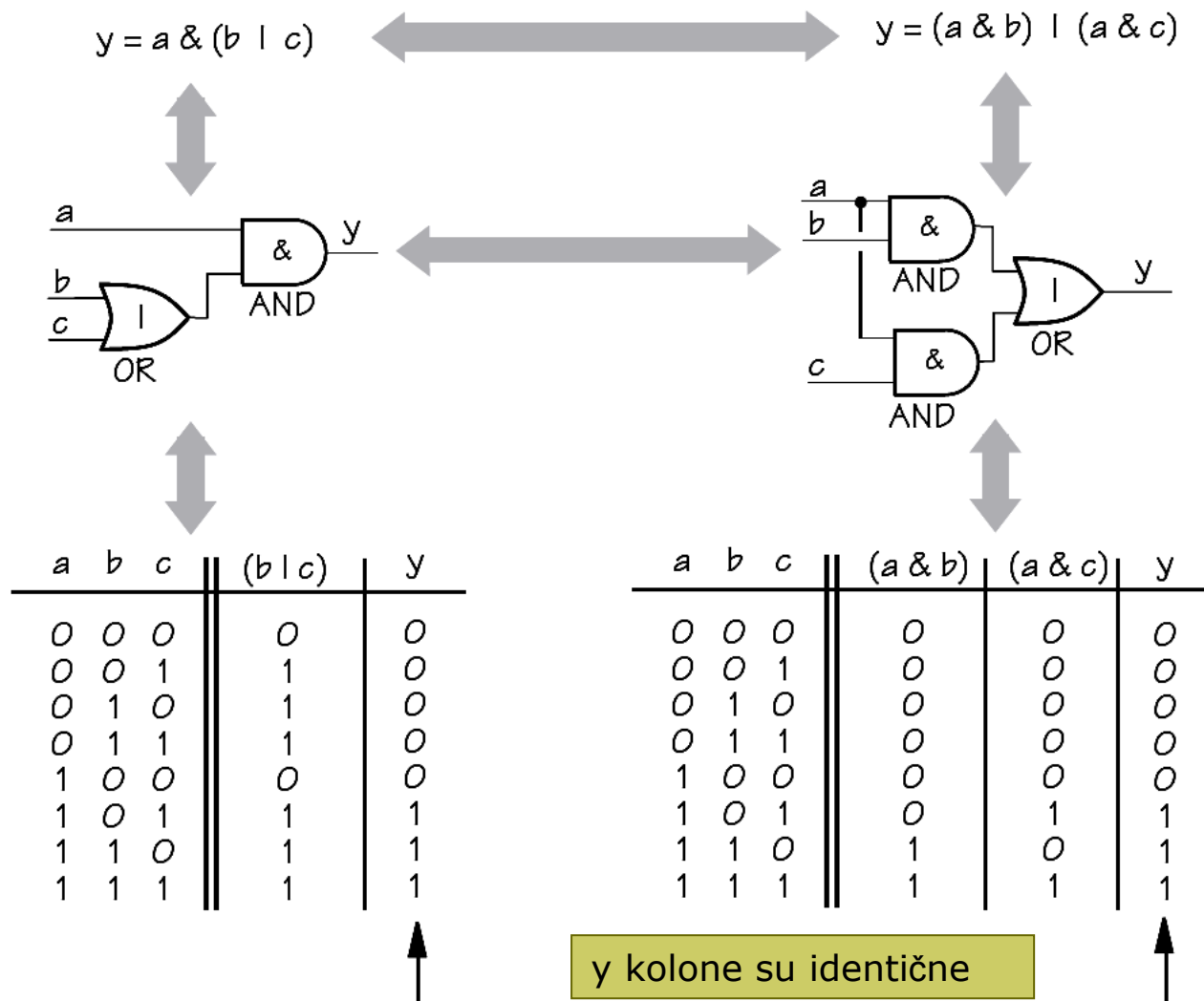

Prednosti


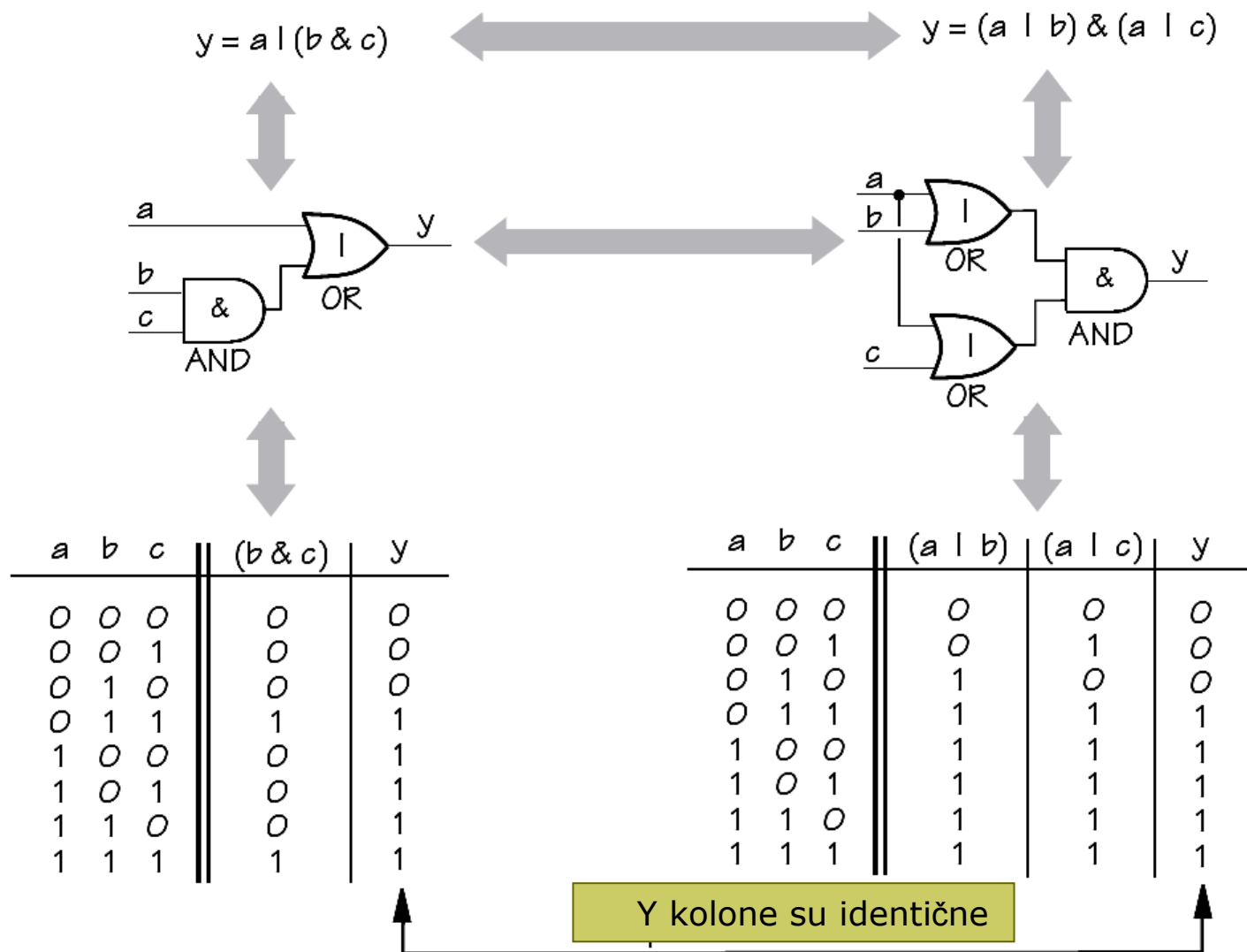


Spec. slučajevi logičkog sabiranja

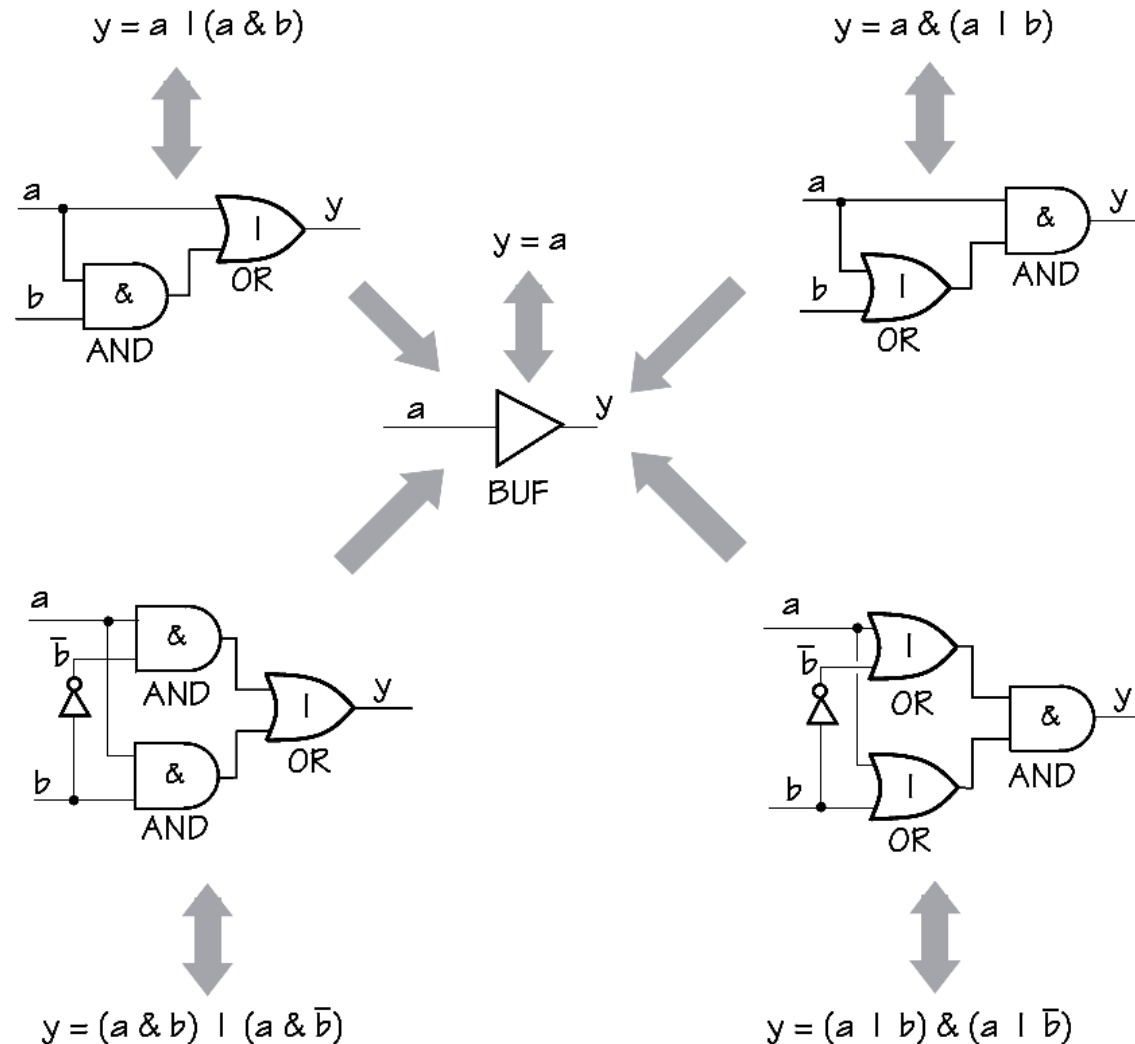



Uprošćavanje log. izraza

$$y = a \mid (\bar{a} \& b)$$

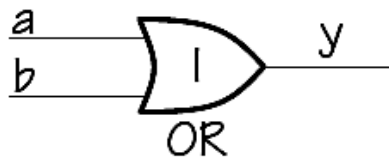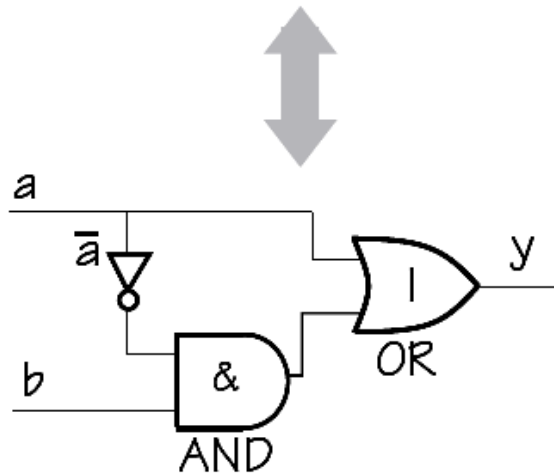

$$y = a \mid b$$


$$y = a \& (\bar{a} \mid b)$$

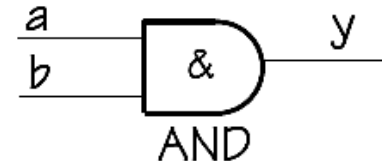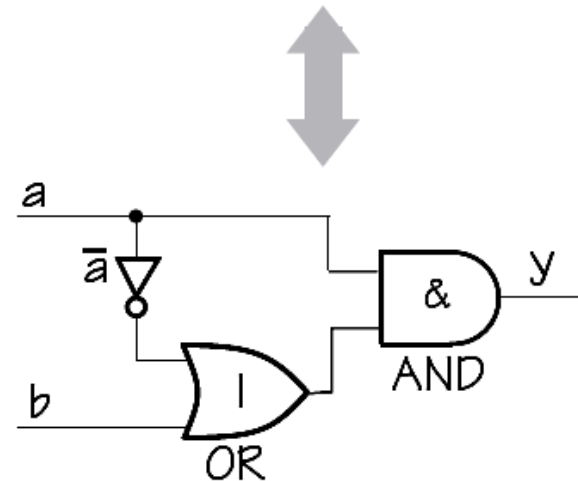

$$y = a \& b$$

Domaći zadatak

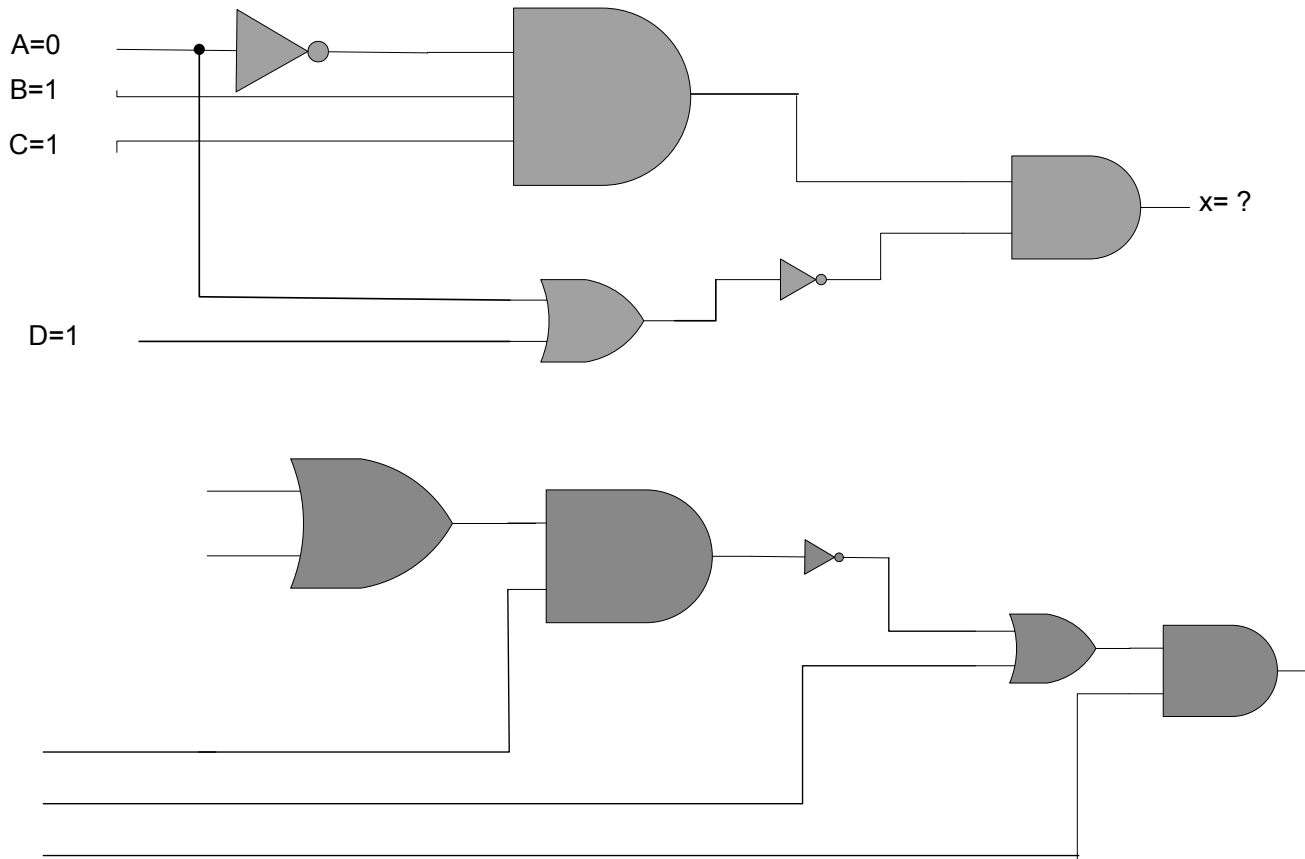- ❑ Odrediti logičko stanje x na izlazu.
- ❑ Napisati logičke funkcije datih kola.




DeMorganovi obrasci





- ❑ *DeMorgano-vi* obrasci **transformišu logičke funkcije**.
- ❑ *DeMorgan-ove transformacije* se satoje od **4 koraka** (stepa):
 1. Izmenite sve **&** operatore sa **|** operatorima i obratno.
 2. Invertujte sve promenljive, takođe izmenite **0** u **1** i obratno.
 3. Invertujte **kompletnu** funkciju.
 4. Redukujte niz **više invertora** (ako postoji).
- ❑ Pogledamo primer primene *DeMorganovih obrazaca* na sledećem slajdu:

$$y = a \ \& \ b$$


2-ulazna I funkcija (1)

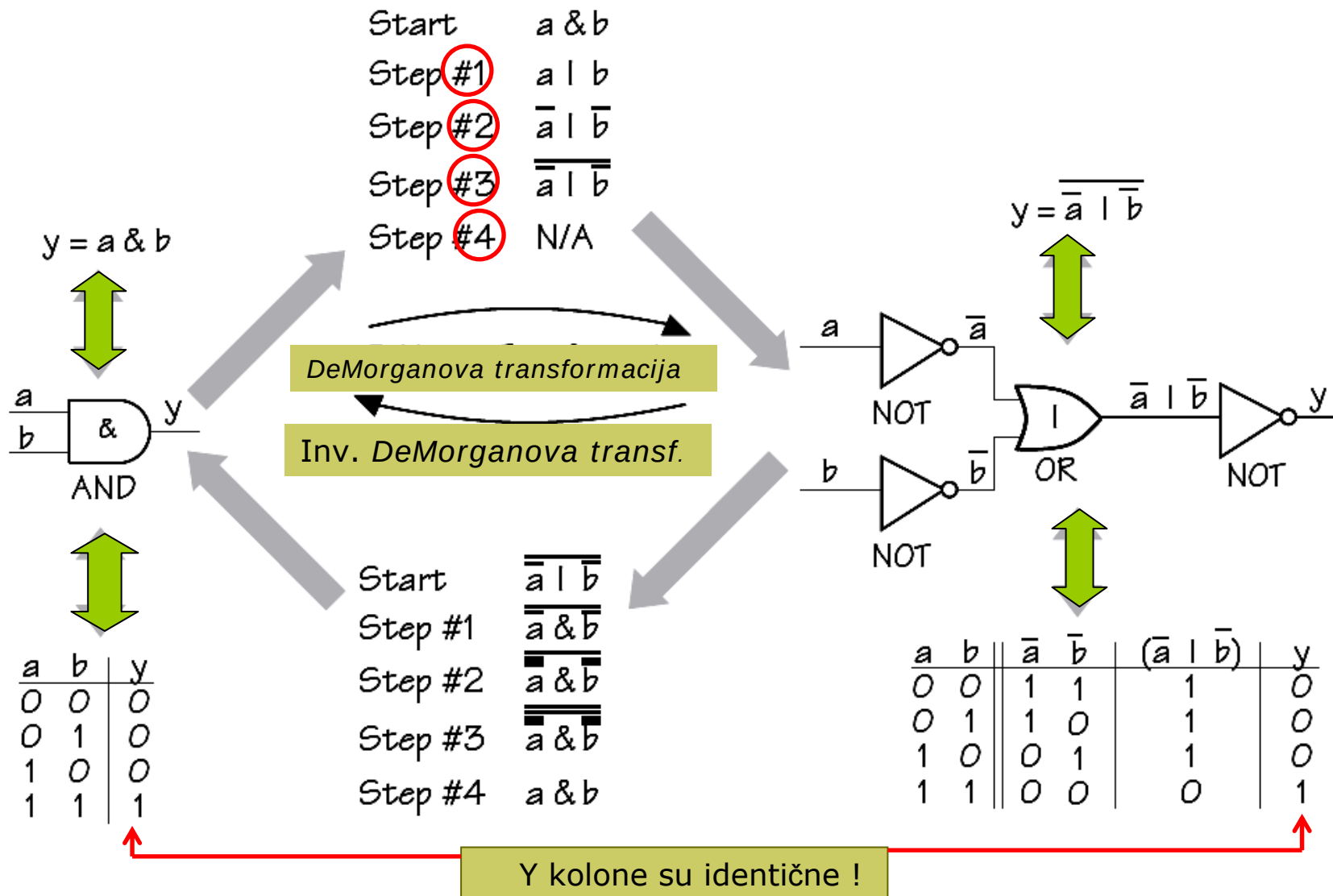



2-ulazna I/NILI funkcija (2)

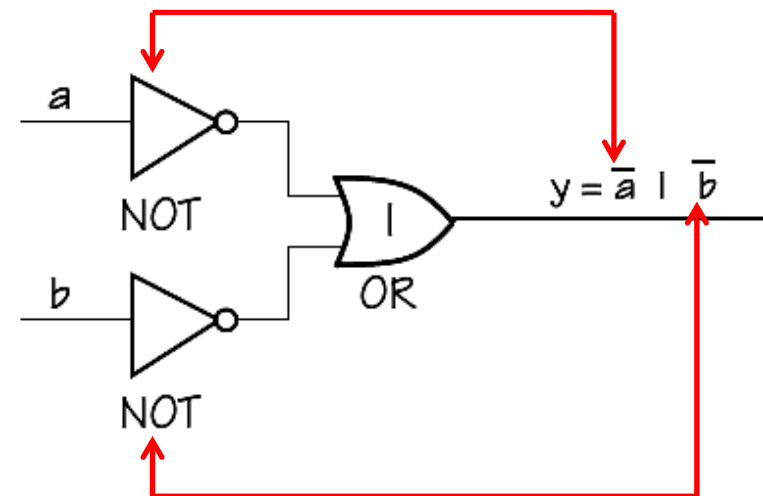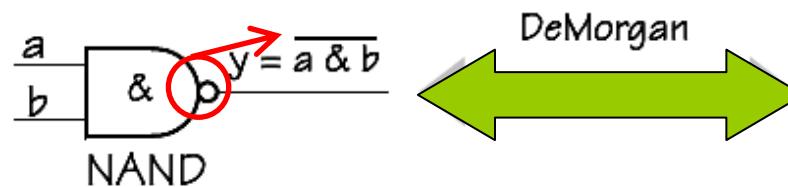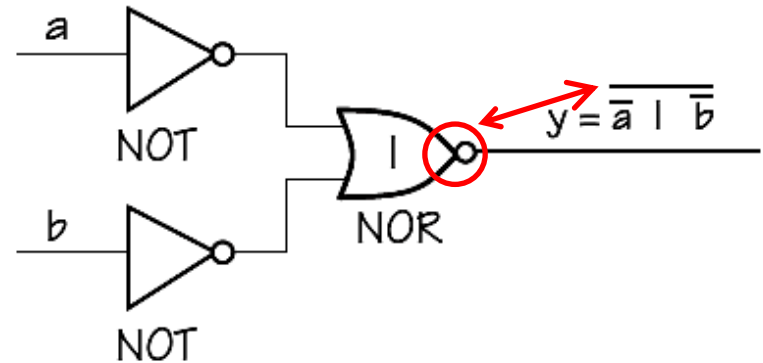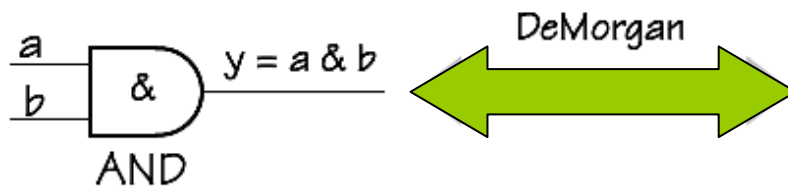


2-ulazna ILI/NILI funkcija

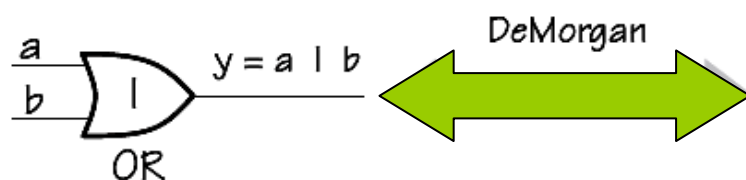

DeMorgan

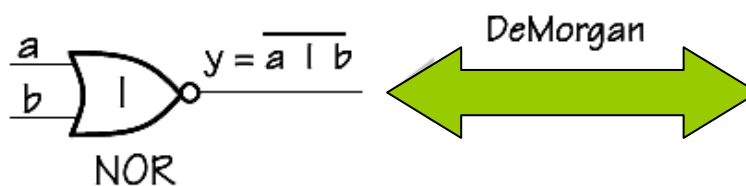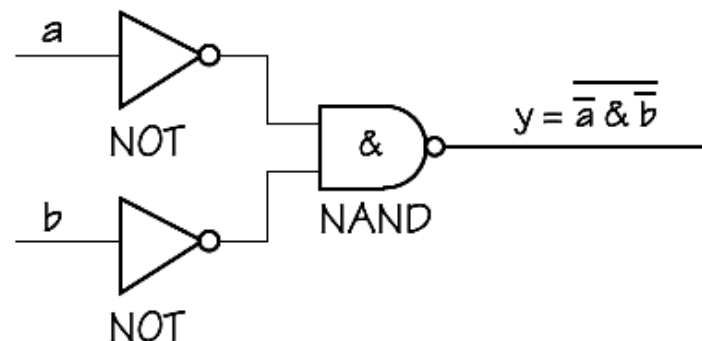

DeMorgan

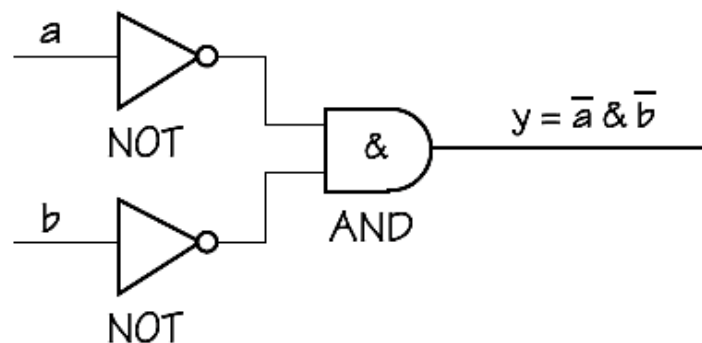

Realizacija Bulovih funkcija


- ❑ U osnovi postoje dve tehnike za realizaciju Bulovih jednačina direktno iz tabele istinitosti.
- ❑ Kod prve tehnike formiraju se **mintermi** za svaku liniju iz tabele istinitosti čiji je izlaz jednak **1** a zatim se povezuju **ILI** operaterom.
- ❑ Ova realizacija se naziva **suma-proizvoda**.
- ❑ Kod druge tehnike formiraju se **maxtermi** za svaku liniju iz tabele istinitosti čiji je izlaz jednak **0** a zatim se povezuju **I** operaterom.
- ❑ Ova realizacija se naziva **proizvod-suma**.

Kanonične forme: minterm, maxterm

<i>a</i>	<i>b</i>	<i>c</i>	mintermi	maxtermi
0	0	0	$(\bar{a} \& \bar{b} \& \bar{c})$	$(a \mid b \mid c)$
0	0	1	$(\bar{a} \& \bar{b} \& c)$	$(a \mid b \mid \bar{c})$
0	1	0	$(\bar{a} \& b \& \bar{c})$	$(a \mid \bar{b} \mid c)$
0	1	1	$(\bar{a} \& b \& c)$	$(a \mid \bar{b} \mid \bar{c})$
1	0	0	$(a \& \bar{b} \& \bar{c})$	$(\bar{a} \mid b \mid c)$
1	0	1	$(a \& \bar{b} \& c)$	$(\bar{a} \mid b \mid \bar{c})$
1	1	0	$(a \& b \& \bar{c})$	$(\bar{a} \mid \bar{b} \mid c)$
1	1	1	$(a \& b \& c)$	$(\bar{a} \mid \bar{b} \mid \bar{c})$




"I" funkcije

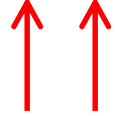


"ILI" funkcije



Dizajn prekidačkih funkcija

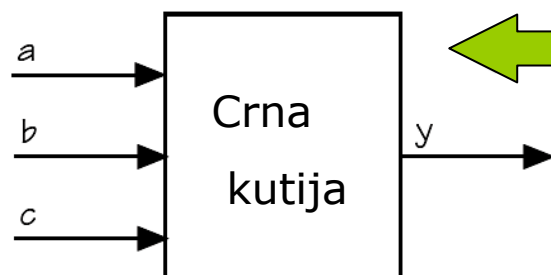

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

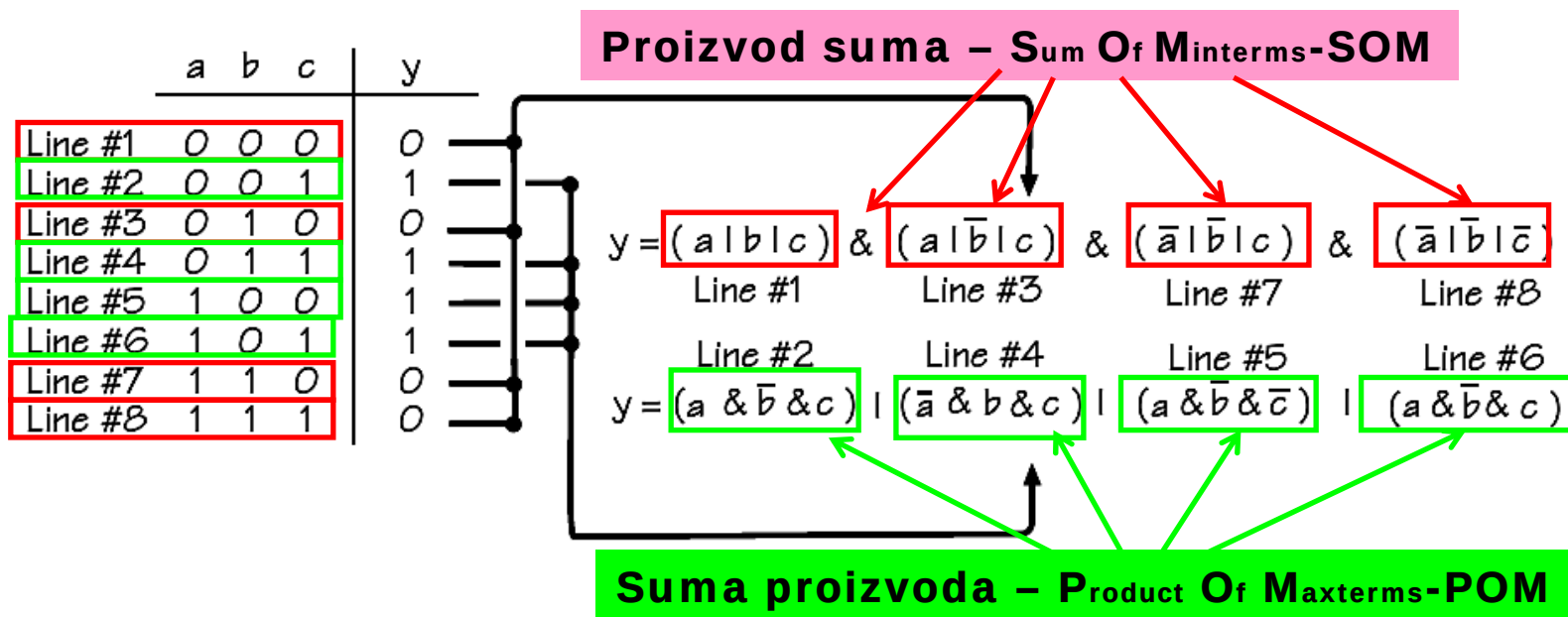

Realizacija prekidačkih funkcija

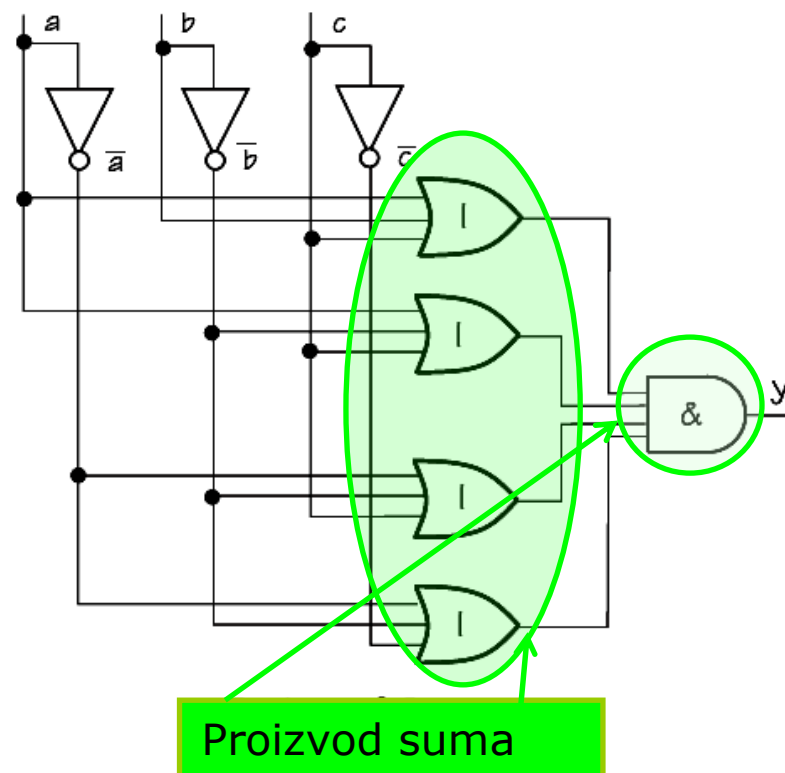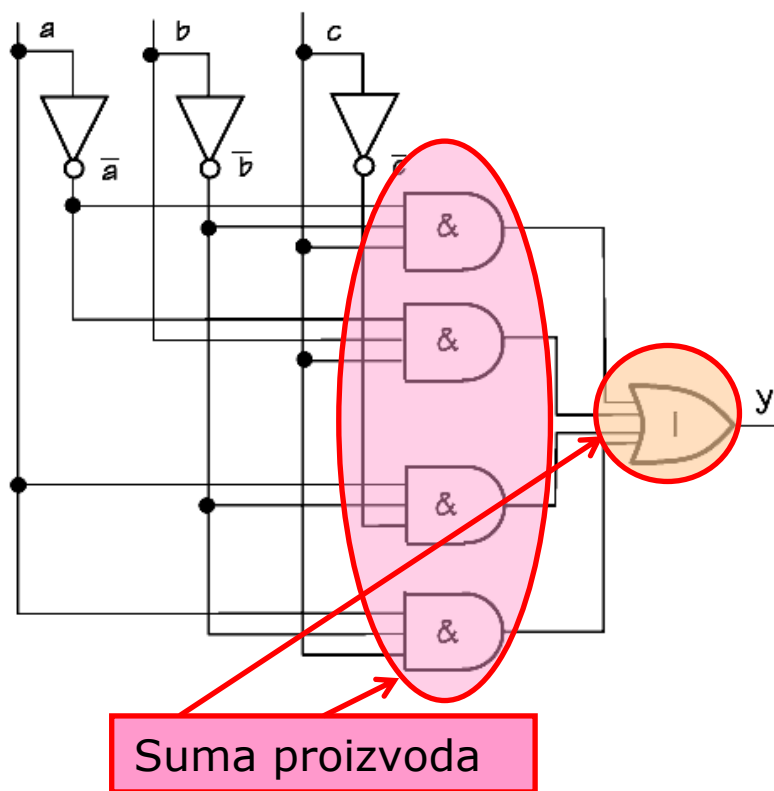

Domaći zadatak

- Realizujte funkciju y predstavljenu tablicom istinitosti:

A	B	C	D	y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1